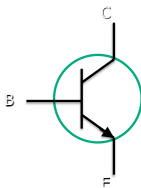




Electronics and Microelectronics AE4B34EM

5. lecture

- Bipolar transistor
- Parameters
- Applications




Transistor

- **Active components** are needed in electronics and microelectronics circuits out of passive components (resistors, capacitors, inductors, ...)
- A **transistor** is a **semiconductor device** used to **amplify** and **switch** electronic signals
- Transistors are made of a solid piece of semiconductor material, with at least three terminals for connection to an external circuit
- The transistors are the fundamental building block of modern electronic devices.



Transistors - types

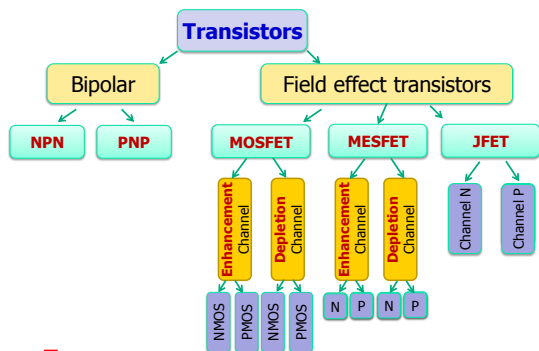


Bipolar transistors

- Consists of 3 alternate layers of *n* and *p* type semiconductor called **emitter** (*E*), **base** (*B*) and **collector** (*C*).
- Majority of current enters collector, crosses base region and exits through emitter. A small current also enters base terminal, crosses base-emitter junction and exits through emitter.



The BJT – Bipolar Junction Transistor

The Two Types of BJT Transistors:

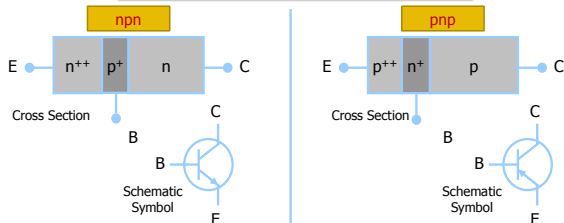


Note: Normally Emitter layer is heavily doped, Base layer is lightly doped and Collector layer has Moderate doping.


Collector doping is usually $\sim 10^{15}$
Base doping is slightly higher $\sim (10^{16} - 10^{17})$
Emitter doping is much higher $\sim 10^{22}$



BJT Current & Voltage - Equations

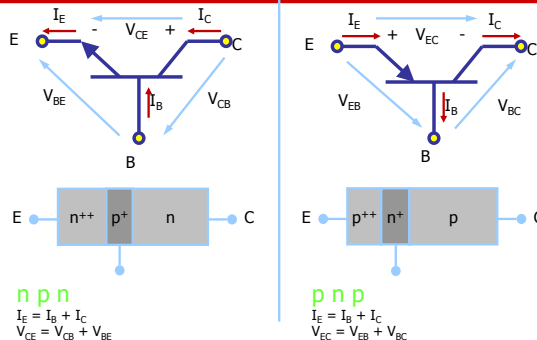


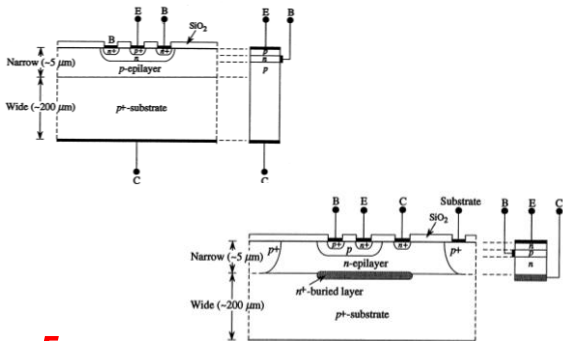Cross sections and simplified models of discrete and IC npn BJTs



Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Physical Structure

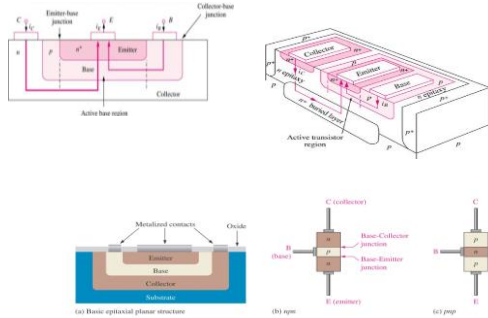


Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Various Regions (Modes) of Operation of BJT

There are four basic operation regions

Region	Polarization B-E	Polarization B-C
Cutoff	$V_{BE} < V_T$ reverse	$V_{BC} < 0$ reverse
Forward-active	$V_{BE} > V_T$ forward	$V_{BC} < 0$ reverse
Reverse	$V_{BE} < 0$ reverse	$V_{BC} > U_T$ forward
Saturation	$V_{BE} > 0$ forward	$V_{BC} > 0$ forward

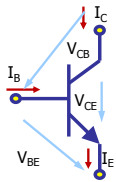

Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Various Regions (Modes) of Operation of BJT

Cutoff: In cutoff, both junctions reverse biased. There is very little current flow, which corresponds to a logical "off", or an open switch.

Forward-active (or simply, **active**): The emitter-base junction is forward biased and the base-collector junction is reverse biased. Most bipolar transistors are designed to afford the greatest common-emitter current gain, β_F , in forward-active mode. If this is the case, the collector-emitter current is approximately proportional to the base current, but many times larger, for small base current variations.


Reverse-active (or **inverse-active** or **inverted**): By reversing the biasing conditions of the forward-active region, a bipolar transistor goes into reverse-active mode. In this mode, the emitter and collector regions switch roles. Since most BJTs are designed to maximize current gain in forward-active mode, the β_F in inverted mode is several times smaller. This transistor mode is seldom used. The reverse bias breakdown voltage to the base may be an order of magnitude lower in this region.

Saturation: With both junctions forward-biased, a BJT is in saturation mode and facilitates current conduction from the emitter to the collector. This mode corresponds to a logical "on", or a closed switch.




Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Two diodes in series






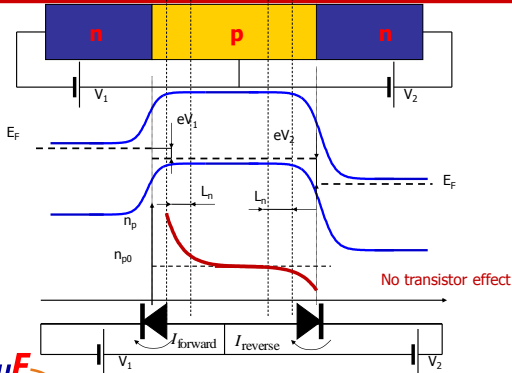


Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Cutoff region $W_B < L_n$

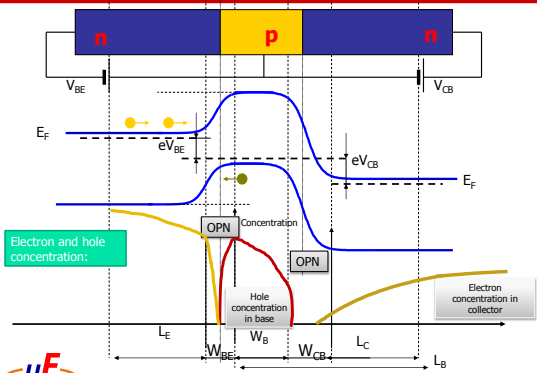

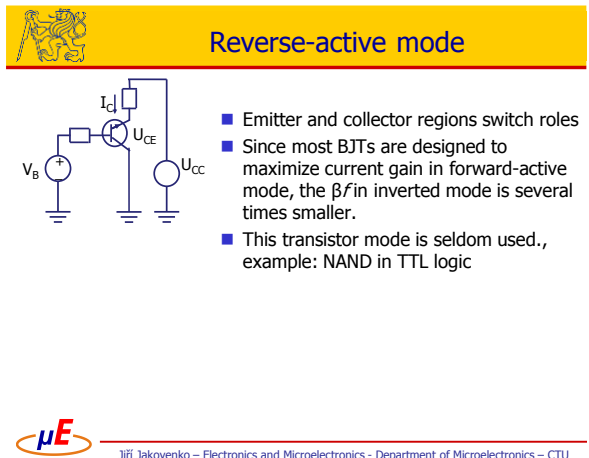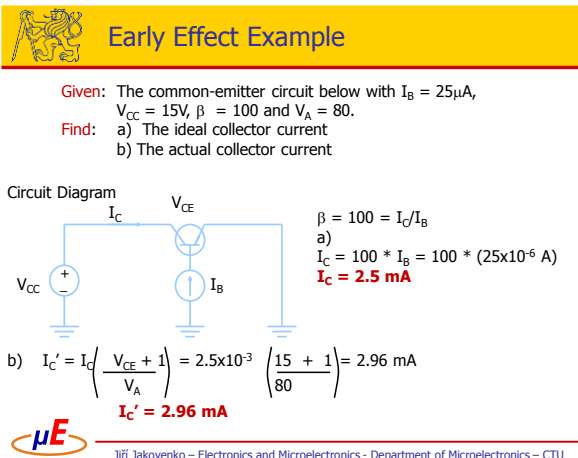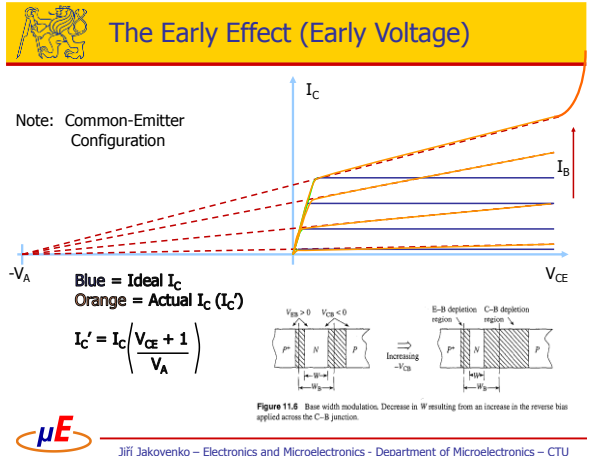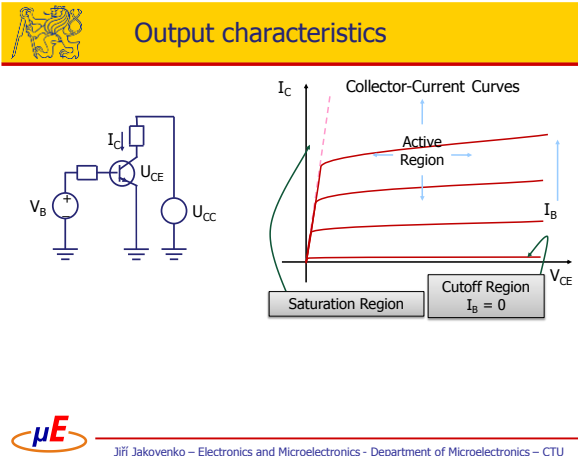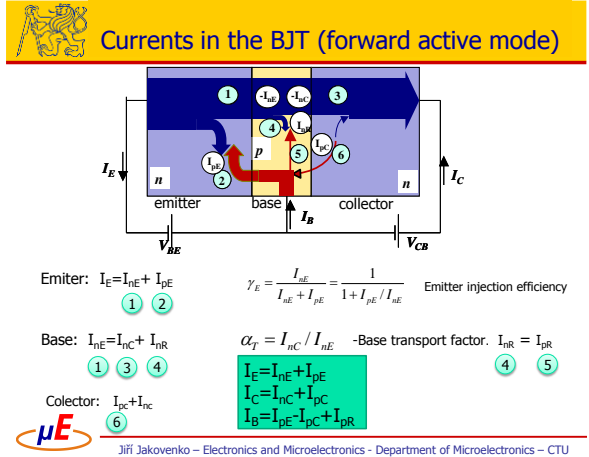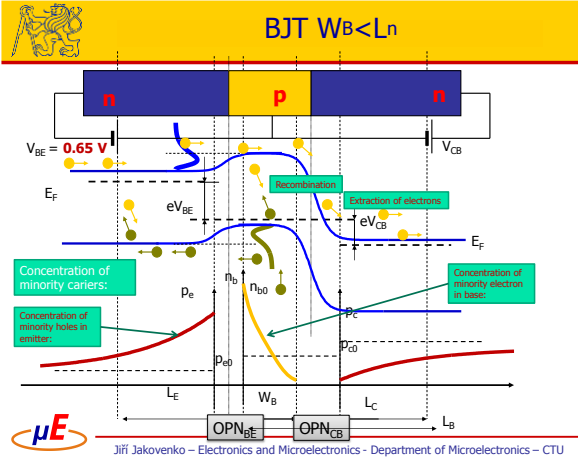Jiří Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU



Saturation mode

- If base current is so large that electron injection causes flooding of BC junction, its polarization will change in a **forward direction**
- Transistor shows very little resistance
- Transistor is used as a switch
- Disadvantage - need to divert off a great charge from the base

μE Jifi Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Input characteristic

Collector Current:
 $I_C = \alpha I_{ES} e^{U_{BE}/U_T}$

Transconductance:
 (slope of the curve)
 $g_m = \Delta I_C / \Delta V_{BE}$

I_{ES} = The reverse saturation current of the B-E Junction.
 $U_T = kT/q = 26 \text{ mV}$ (@ $T=300 \text{ K}$)
 η = the emission coefficient and is usually ~ 1

μE Jifi Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Boundary parameters

- Max. voltage V_{CE}
- Max. voltage V_{BE}
- Max. current I_C
- Max. power dissipation $P_{C_{MAX}} = V_{CE} \cdot I_C$
- Max. input current I_B

μE Jifi Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Basic BJT circuits

Biasing the transistor refers to applying voltages to the transistor to achieve certain operating conditions:

1. Common-Base Configuration (CB): input = V_{EB} & I_E
output = V_{CB} & I_C
2. Common-Emitter Configuration (CE): input = V_{BE} & I_B
output = V_{CE} & I_C
3. Common-Collector Configuration (CC): input = V_{BC} & I_B
(Also known as Emitter follower) output = V_{EC} & I_E

μE Jifi Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Common-Base (CB) Characteristics

μE Jifi Jakovenko – Electronics and Microelectronics - Department of Microelectronics – CTU

Common-Base (CB) Characteristics

- α = Common-base current gain
- (0.9-0.999; typical 0.99)


$$\alpha = \frac{i_C}{i_E}$$

$$i_C = I_S e^{U_{BE}/U_T}$$

$$i_E = \frac{I_S}{\alpha} e^{U_{BE}/U_T}$$

μE Jifi Jakovenko – Elektronika a Mikroelektronika - Katedra mikroelektroniky – ČVUT FEL

Common-Emitter Configuration (CE)

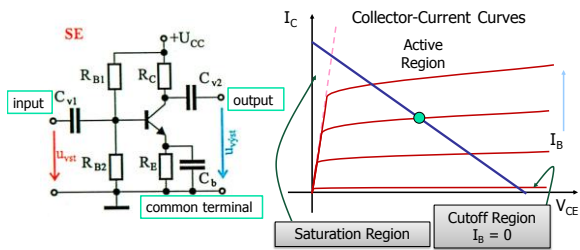


Common-Emitter Configuration (CE)

- β = Common-emitter current gain (10-1000; typical 50-200)


$$\beta = \frac{i_C}{i_B}$$

$$i_C = I_S e^{U_{BE}/U_T}$$
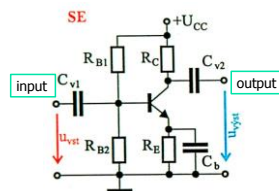
$$i_B = \frac{I_S}{\beta} e^{U_{BE}/U_T}$$



Common-Collector Configuration

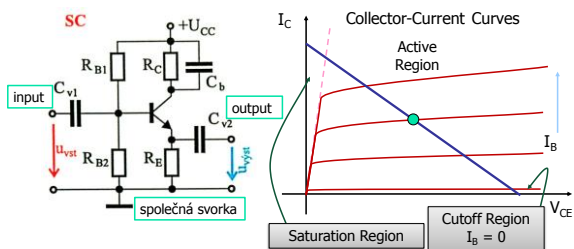

The Common-Collector biasing circuit is basically equivalent to the common-emitter biased circuit except instead of looking at I_C as a function of V_{CE} and I_B we are looking at I_E . Also, since $\alpha \sim 1$, and $\alpha = I_C/I_E$ that means $I_C \sim I_E$



Relation between α and β

- α = Common-base current gain
- β = Common-emitter current gain

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Example:
 $\alpha = 0.98, \beta = 49$
 $\alpha = 0.99, \beta = 99$
 $\alpha = 0.995, \beta = 199$

