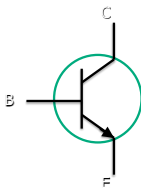





Electronics and Microelectronics AE4B34EM

6. lecture


- Bipolar transistor
- Parameters
- Applications



Circuit variation

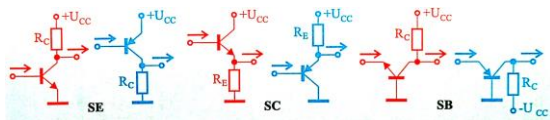

Amlifiers

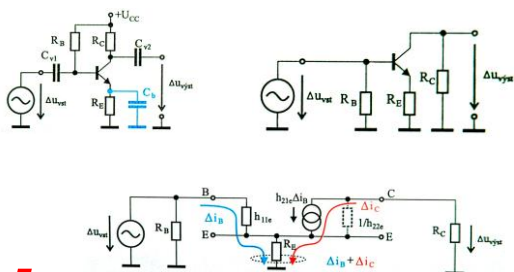

Linear model and h parameters



$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

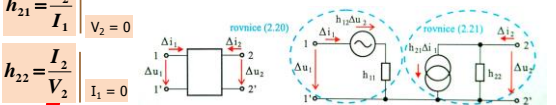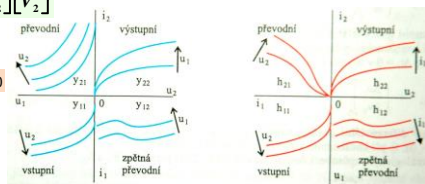

h - Parameters


$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

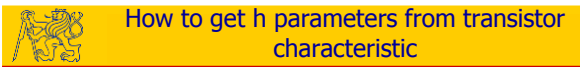- $h_{11} = h_i$ = Input Resistance
- $h_{12} = h_r$ = Reverse Transfer Voltage Ratio
- $h_{21} = h_f$ = Forward Transfer Current Ratio
- $h_{22} = h_o$ = Output Admittance




How to get h parameters from transistor characteristic


$$h_{11e} = \frac{\Delta V_{BE}}{\Delta I_B} \Big|_{\Delta I_{CE}=0}$$

$$h_{21e} = \frac{\Delta I_C}{\Delta I_B} \Big|_{\Delta V_{CE}=0}$$

$$h_{22e} = \frac{\Delta I_C}{\Delta V_{CE}} \Big|_{\Delta I_B=0}$$

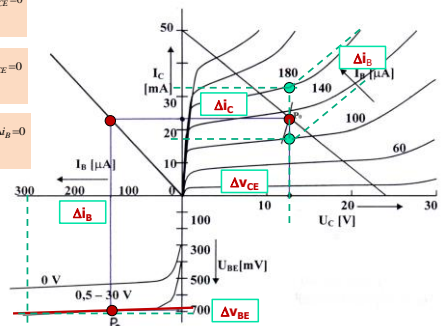

BJT Amplifiers

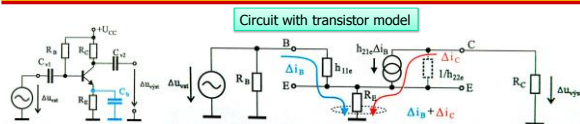

- 1. Solution without capacitance C_B
- For simplicity, we neglect h_{21e} and h_{22e}


$$\Delta u_{vyst} = -h_{21e} \cdot \Delta i_B \cdot R_C$$

$$\Delta u_{vst} = h_{11e} \cdot \Delta i_B + R_E \cdot (\Delta i_B + h_{21e} \cdot \Delta i_B) = [h_{11e} + R_E \cdot (1 + h_{21e})] \Delta i_B$$

- Voltage gain:

$$A_u = \frac{\Delta v_{vyst}}{\Delta v_{vst}} = - \frac{h_{21e} \cdot R_C}{h_{11e} + R_E \cdot (1 + h_{21e})}$$

BJT Amplifiers

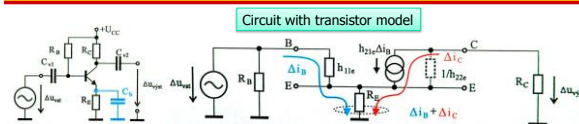

- For $h_{11e} \ll R_E \cdot (1 + h_{21e})$


$$A_v = \frac{\Delta v_{vyst}}{\Delta v_{vst}} = - \frac{R_C}{R_E}$$

- 2. With capacitance:

$$A_u = \frac{\Delta v_{vyst}}{\Delta v_{vst}} = - \frac{h_{21e} \cdot R_C}{h_{11e}}$$

BJT amplifier - example

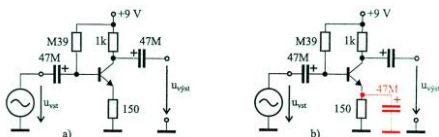
- Calculate voltage gain. Given: h_{21e} 200 and h_{22e} 600 Ohm



$$A_u = \frac{\Delta v_{vyst}}{\Delta v_{vst}} = - \frac{R_C}{R_E} = \frac{1000}{150} = -6,67$$

$$A_u = \frac{\Delta v_{vyst}}{\Delta v_{vst}} = - \frac{h_{21e} \cdot R_C}{h_{11e}} = \frac{200 \cdot 1000}{600} = -333$$

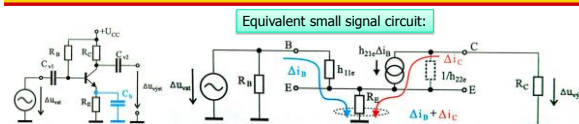BJT amplifier – input and output resistance



- C_b is included:

$$R_{vst} = R_B \parallel h_{11e}$$

- C_b is excluded:


$$R_{vst} = R_B \parallel \left(\frac{\Delta v_{vst}}{\Delta i_B} \right)^{\Delta v_{vst}=0} = R_B \parallel [h_{11e} + R_E (1 + h_{21e})]$$

- Output resistance:


$$R_{vyst} = (1/h_{22e}) \parallel R_C$$

Common collector and base circuits and equivalent small signal models

- Common collector circuit

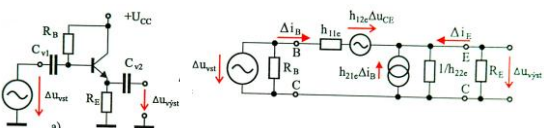


- Common base circuit

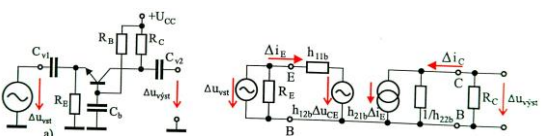



Properties of BJT amplifiers

Parametr	SE	SC	SB
A_u	$-(h_{21e}/h_{11e}) \cdot (R_C \parallel 1/h_{22e})$ velké menší než 1	$(h_{21e} \cdot R_E) / (h_{21e} \cdot R_E + h_{11e})$	$(h_{21e}/h_{11e}) \cdot (R_C \parallel 1/h_{22e})$ velké
A_i	$h_{21e} \gg 1$	$h_{21e} \gg 1$	$[h_{21e} / (1 + h_{22e} \cdot R_C)] < 1$
$A_P = A_v \cdot A_u$	velké	malé	malé
R_{vst}	$R_B \parallel h_{11e}$ střední	$R_B \parallel [h_{11e} + (h_{21e} + 1) \cdot R_E]$ velký	$R_E \parallel h_{11e}$ malý
R_{vyst}	$R_C \parallel (1/h_{22e})$ střední	$R_E \parallel [(h_{11e} + R_B) / h_{21e}]$ malý	$R_C \parallel (1/h_{22e})$ velký


The lower and upper limit frequency

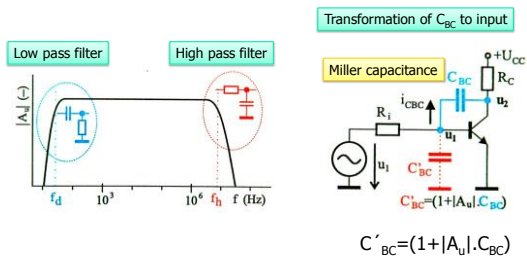

Amplifier class A and B

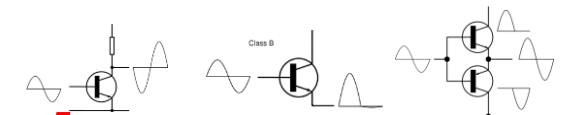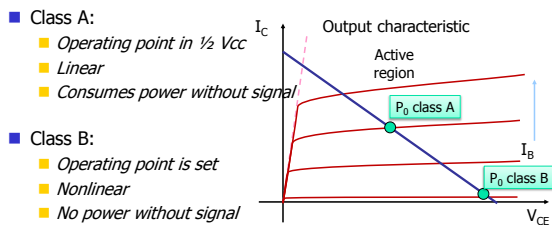

Amplifier class A and B

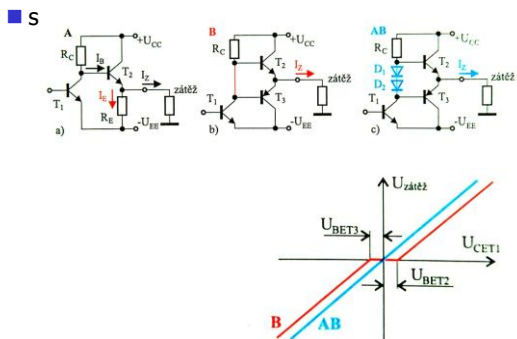

BJT as a switch

- Switch with ohmic load

